

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN ELECTRONICS ENGINEERING & EMBEDDED SYSTEM – CP04
II SEMESTER REGULAR & SUPPLEMENTARY EXAMINATION-JUNE 2023

Subject: Digital Electronics-I
Subject Code: CP04205T

Total Time: 2 Hr.
Total Marks: 50

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING **2*8=16**

- 1.1 Classify ICs in different Integration Levels.
- 1.2 Define the following terms related to Binary Information:
 - a) Word
 - b) Double Word
- 1.3 Find the 10's complement of (456).
- 1.4 Define the terms Fan-in & Fan-out
- 1.5 Define Combinational Circuits
- 1.6 Define Multiplexer. Draw the block diagram of Multiplexer.
- 1.7 List the applications of CMOS.
- 1.8 Define Encoder & Encoding
- 1.9 Find the 2's complement of (1101).
- 1.10 Define Rise time and fall time

2.0 ANSWER ANY SIX OF THE FOLLOWING **3*6=18**

- 2.1 How digital circuits are important over analog circuits?
- 2.2 Define Gate Propagation Delay
- 2.3 Prove that $(A + AB) = A$
- 2.4 Implement NOT Logic, OR Logic, & AND Logic using NOR logic gates only.
- 2.5 Draw the logic circuit for 1-bit Comparator & write the truth table for the same.
- 2.6 Explain the 1:4 Demultiplexer with neat block diagram & logic circuit.
- 2.7 Define Multivibrator. List the modes of operation of IC 555 Timer
- 2.8 List the advantages & disadvantages of TTL.

3.0 ANSWER ANY FOUR OF THE FOLLOWING **4*4=16**

- 3.1 Draw the internal block diagram of IC 555 Timer & list the applications
- 3.2 Explain how monostable mode is known as one shot multivibrator?
- 3.3 Define the following terms related to pulse waveforms:
 - a) Amplitude
 - b) Time Period
 - c) Frequency
 - d) Duty Cycle
- 3.4 Minimize the given 3-variable SoP expression using Karnaugh Map
$$Y = \overline{A}BC + \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C}$$
- 3.5 Explain 8:3 Priority Encoder with neat sketch
- 3.6 Draw the logic symbol & truth tables of basic logic gates

