

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN ELECTRONICS ENGINEERING & EMBEDDED SYSTEM – CP04
III SEMESTER REGULAR & SUPPLEMENTARY EXAMINATION-JAN 2023

Subject: Analog Electronics-II
Subject Code: CP04301T

Total Time: 2 Hr.
Total Marks: 50 Marks

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING **2*8=16**

- 1.1 Name different types of transistor biasing circuits.
- 1.2 What is voltage gain?
- 1.3 Draw the symbol of op amp
- 1.4 What is filter and write its type?
- 1.5 Draw the block diagram of Oscillator
- 1.6 What do you mean by cross over distortion?
- 1.7 Draw the voltage follower circuit
- 1.8 Briefly explain the power amplifier with block diagram
- 1.9 Define Slew rate
- 1.10 Explain the concept of thermal resistance

2.0 ANSWER ANY SIX OF THE FOLLOWING **3*6=18**

- 2.1 Explain DC load line with the help of a diagram
- 2.2 What do you mean by zero crossing detector? Explain with neat sketch
- 2.3 Explain differentiator with neat circuit diagram.
- 2.4 Draw and explain PWM generation using op amp
- 2.5 Differentiate class A, class B and class AB power amplifier
- 2.6 List out the applications of filter
- 2.7 Explain the working of Hartley oscillator with neat diagram
- 2.8 Draw the circuit of subtractor by using double inversion method

3.0 ANSWER ANY FOUR OF THE FOLLOWING **4*4=16**

- 3.1 Draw and explain about instrumentation amplifier by using three op amp
- 3.2 Draw and explain the working of RC phase shift oscillator circuit
- 3.3 Explain with circuit diagram of emitter follower as voltage regulator
- 3.4 Draw & explain the block diagram of Op amp
- 3.5 Design A non-inverting amplifier for $A_v=10$ & $V_{in}=2V$ $R_1=1K$ & find V_{out}
- 3.6 Draw and explain the Schmitt trigger circuit

