

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN ELECTRONICS ENGINEERING & EMBEDDED SYSTEM – CP04
III SEMESTER REGULAR & SUPPLEMENTARY EXAMINATION-JAN 2023

Subject: Digital Electronics-II
Subject Code: CP04302T

Total Time: 2 Hr.
Total Marks: 50 Marks

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING **2*8=16**

- 1.1 Define Sequential Circuits
- 1.2 List the alternate names for Johnson Counter.
- 1.3 Define Counters & Brief about need for Counters.
- 1.4 Define Bidirectional Shift Registers.
- 1.5 Define Data Conversion. List the types of Data Converters.
- 1.6 List the Units of Binary Data
- 1.7 List the 3 parameters which can determine the performance of memory system
- 1.8 Write a short note on Flash Memory.
- 1.9 Classify Analog to Digital Converters.
- 1.10 Name the 2 types of LED Seven Segment Display

2.0 ANSWER ANY SIX OF THE FOLLOWING **3*6=18**

- 2.1 Define Triggering & What are the types of triggering?
- 2.2 Explain the working of 4-bit SISO Shift Register with neat sketch
- 2.3 Write the comparison between combinational circuits & sequential circuits.
- 2.4 Differentiate between Binary Weighted DAC & R-2R Ladder DAC.
- 2.5 Define the following parameters related to performance of memory system.
a) Access Time b) Memory Cycle Time c) Transfer Rate
- 2.6 Write a short note on EEPROM.
- 2.7 Define PAL. Explain the working of PAL with neat block diagram
- 2.8 Explain the working of common cathode SSD with neat circuit diagram

3.0 ANSWER ANY FOUR OF THE FOLLOWING **4*4=16**

- 3.1 Differentiate between asynchronous counters & synchronous counters
- 3.2 Explain the working of MOD-10 Ripple Up Counter with neat sketch
- 3.3 Design a 4-bit Johnson Counter using D Flip-flop.
- 3.4 List the advantages & disadvantages of single slope or ramp type ADC.
- 3.5 Compare CPLDs to FPGAs.
- 3.6 Define PLA. Explain with the neat block diagram, the working of PLA

