

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN COMPUTER ENGINEERING & IT INFRASTRUCTURE – CP08
II SEMESTER REGULAR & SUPPLEMENTARY EXAMINATION-JULY 2023

Subject: Applications of Analog & Digital Circuits
Subject Code: CP082056T

Total Time: 2 Hr.
Total Marks: 50

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING

2*8=16

- 1.1 Draw the symbol of transistor and mark three region.
- 1.2 How many contacts does relay have? Name them
- 1.3 List out the types of MOSFET
- 1.4 Draw the diagram of Open drain configuration
- 1.5 Define Multiplexer. List out the applications of multiplexer.
- 1.6 Define shift register
- 1.7 Define the terms alpha & beta
- 1.8 What are the Characteristics of Logic Family?
- 1.9 Name the types of Data Converter
- 1.10 List out the applications of counters

2.0 ANSWER ANY SIX OF THE FOLLOWING

3*6=18

- 2.1 Explain how conduction is initiated in NPN transistor?
- 2.2 Explain the working of transistor as a switch with neat diagram
- 2.3 Draw the structure of N- channel enhancement type MOSFET
- 2.4 Write down the limitations of Totem pole output?
- 2.5 Design 4:1 multiplexer circuit with neat diagram
- 2.6 Differentiate between BJT and MOSFET.
- 2.7 Define Fan in & Fan out
- 2.8 Draw the block diagram of ADC process

3.0 ANSWER ANY FOUR OF THE FOLLOWING

4*4=16

- 3.1 Write the comparison between 3 configurations of transistor
- 3.2 Differentiate between Asynchronous and Synchronous counter
- 3.3 Explain about 4 bit SISO with neat sketch
- 3.4 Explain binary weighted type DAC with neat sketch
- 3.5 Draw the construction details of P type enhancement MOSFET and show the biasing details.
- 3.6 List down the classifications of semiconductor memories

