

**NETTUR TECHNICAL TRAINING FOUNDATION**  
**DIPLOMA IN MECHATRONICS ENGINEERING & SMART FACTORY-CP15**  
**III SEMESTER REGULAR & SUPPLEMENTARY EXAMINATION-JAN 2023**

**Subject: Industrial electronics**  
**Subject Code: CP15304T**

**Total Time: 2 Hr.**  
**Total Marks: 50 Marks**

**PART B**

**1.0 ANSWER ANY EIGHT OF THE FOLLOWING** **2\*8=16**

- 1.1 List out any four applications of power electronics
- 1.2 Draw the symbol of SCR and mark its terminals
- 1.3 List out any 3 applications of GTO
- 1.4 How protection circuits helps to safe guard the devices?
- 1.5 List out any 4 applications of chopper
- 1.6 List out the types of DC-DC converters.
- 1.7 Write the different methods to control the output of inverter
- 1.8 What are the different types of Cycloconverters?
- 1.9 Name the different methods to control the speed of AC motor
- 1.10 List out 4 applications of pulse circuit using SCR.

**2.0 ANSWER ANY SIX OF THE FOLLOWING** **3\*6=18**

- 2.1 List out any four difference between normal diode and power diode.
- 2.2 How latching current and holding current can be differentiated.
- 2.3 Draw and explain the circuit diagram of Buck converter
- 2.4 Explain in detail about the classification of inverter.
- 2.5 With a neat block diagram, explain the working principle of V/F control.
- 2.6 Draw and explain the block diagram of a linear power supply.
- 2.7 Elaborate the role of SCR in a fully controlled bridge rectifier.
- 2.8 How DC is converted to AC in single phase half wave inverter?

**3.0 ANSWER ANY FOUR OF THE FOLLOWING** **4\*4=16**

- 3.1 Draw the structure of IGBT and explain its working
- 3.2 Draw the V-I characteristics of TRIAC and mark the forward conduction region.
- 3.3 Draw the circuit diagram and explain the working of a single phase cyclo converter.
- 3.4 With a neat block diagram, explain the working of SMPS circuits.
- 3.5 Explain about various braking modes of DC drives
- 3.6 Explain the different types of UPS

**NETTUR TECHNICAL TRAINING FOUNDATION**  
**DIPLOMA IN MECHATRONICS - CP15**  
**III SEMESTER SUPPLEMENTARY EXAMINATION – JAN 2023**

**Subject: Measuring System**  
**Subject Code: CP15 03 05**

**Total Marks : 50**  
**Total Time : 2H**

**PART B**

- 1.0 ANSWER ANY EIGHT OF THE FOLLOWING** **2\*8=16**
1. 1 Define the following: a) Absolute Pressure b) Vacuum Pressure
  1. 2 What is the need of measuring system?
  1. 3 Draw the various shapes of the bourdon tubes.
  1. 4 What is Diaphragm?
  1. 5 Write a short note on LM2907
  1. 6 What is true value?
  1. 7 Design a voltage to frequency converter for output frequency of 5KHz.
  1. 8 Write a short note on D.C Tachometer
  1. 9 Define temperature.
  1. 10 What are the limitation of load cell?
- 2.0 ANSWER ANY SIX OF THE FOLLOWING** **3\*6=18**
2. 1 List LM2907 advantages & applications
  2. 2 Write short notes on Bellows
  2. 3 Draw neat diagram of Bimetallic strips explain its working.
  2. 4 What is reluctance pressure transducers? Name its types.
  2. 5 List the features of 8038 IC
  2. 6 What is digital shaft encoder?
  2. 7 Explain about AD590 & LM35
  2. 8 Write short notes on calibration
- 3.0 ANSWER ANY FOUR OF THE FOLLOWING** **4\*4=16**
3. 1 List different types of mechanical tachometer & explain anyone
  3. 2 Explain about potentiometric pressure transducers
  3. 3 Explain Working of thermocouple and its types
  3. 4 Draw and explain the functional block diagram of IC8038.
  3. 5 Explain principle, operation and Application of LVDT for displacement measurement
  3. 6 Explain how diodes can be used as a temperature sensor with neat sketch