

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN MECHATRONICS ENGINEERING & SMART FACTORY – CP15
IV SEMESTER REGULAR & SUPPLEMENTARY EXAMINATION-JULY 2023

Subject: Programmable Logic Controller-I

Total Time: 2 Hr.

Subject Code: CP15404T

Total Marks: 50

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING

2*8=16

- 1.1 Write a short notes on importance of PLC role in automation.
- 1.2 List out the different types of programming languages in PLC
- 1.3 Write any 4 digital input device names.
- 1.4 Draw a PLC ladder diagram for OR gate with truth table.
- 1.5 What is a register? List out the different registers in PLC.
- 1.6 Draw the block format of timer and label it.
- 1.7 List the various types of comparison functions in PLC.
- 1.8 Brief JUMP instruction. Mention the types.
- 1.9 Mention the functions used for changing the BIT STATUS
- 1.10 List out the types of shift register functions

2.0 ANSWER ANY SIX OF THE FOLLOWING

3*6=18

- 2.1 List out the advantages and disadvantages of PLC
- 2.2 Mention proper construction format of ladder diagram with example diagrams.
- 2.3 Draw the PLC ladder diagram for Motor forward-reverse with mutual interlock
- 2.4 Explain PLC input group register
- 2.5 List the types of counters and explain any one
- 2.6 Write the difference between SKIP and MCR function
- 2.7 Mention 3 types of data movement instructions
- 2.8 Explain PLC input module with neat sketch.

3.0 ANSWER ANY FOUR OF THE FOLLOWING

4*4=16

- 3.1 Explain each part of PLC with the block diagram
- 3.2 Define Register to Table & Table to register function.
- 3.3 Mention different types of timers based on inputs and explain each with example
- 3.4 Explain block transfer function in PLC
- 3.5 Draw the ladder diagram for universal gates.
- 3.6 List the factors considered while selecting a PLC

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN MECHATRONICS ENGINEERING & SMART FACTORY – CP15
IV SEMESTER SUPPLEMENTARY EXAMINATION-JULY 2023

Subject: Industrial Electronics
Subject Code: CP150401

Time: 2 Hr.
Marks: 50

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING

2*8=16

- 1.1 List out any four PPEs
- 1.2 Describe Power Diode
- 1.3 Define softness factor.
- 1.4 List out some of the controlled power devices.
- 1.5 Draw single phase half wave rectifier circuit.
- 1.6 Write short notes on firing angle or triggering angle of an SCR.
- 1.7 List out the types of DC-DC converters.
- 1.8 Write a short notes about snubber circuit
- 1.9 Give the concept of thermal resistance.
- 1.10 Write short notes on EMC

2.0 ANSWER ANY SIX OF THE FOLLOWING

3*6=18

- 2.1 Write the first aid steps taken when a person got heart attack.
- 2.2 Define reverse recovery time.
- 2.3 Draw the symbol of POWER MOSFET and name its terminals
- 2.4 Define Holding & Latching current
- 2.5 What do you mean by duty cycle?
- 2.6 Write the importance of heat sink in a circuit.
- 2.7 Draw the block diagram of DC Drive.
- 2.8 With a neat sketch explain about linear power supplies.

3.0 ANSWER ANY FOUR OF THE FOLLOWING

4*4=16

- 3.1 Explain the term 5S.
- 3.2 List out the applications of power electronics.
- 3.3 Draw and explain the switching characteristics of power BJT
- 3.4 Explain the function of freewheeling diode in rectifier.
- 3.5 Explain the working of buck converter with the help of a neat diagram
- 3.6 Explain about PMDC motor with neat sketch.

