

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN MECHATRONICS ENGINEERING & SMART FACTORY – CP15
IV SEMESTER REGULAR & SUPPLEMENTARY EXAMINATION-JULY 2023

Subject: Programmable Logic Controller-I
Subject Code: CP15404T

Total Time: 2 Hr.
Total Marks: 50

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING

2*8=16

- 1.1 Write a short notes on importance of PLC role in automation.
- 1.2 What is isolation in PLC?
- 1.3 Briefly explain the terms NO, NC with symbols.
- 1.4 Draw a PLC ladder diagram for AND gate with truth table.
- 1.5 Draw the ladder diagram for the Boolean expression $(I1)(I2+I3)(I4.I5) = P$
- 1.6 Briefly explain about holding register.
- 1.7 List out the types of PLC arithmetic functions
- 1.8 Brief JUMP instruction. Mention the types.
- 1.9 Mention the functions used for changing the BIT STATUS
- 1.10 Expand FIFO, LIFO, FAL,CLR.

2.0 ANSWER ANY SIX OF THE FOLLOWING

3*6=18

- 2.1 Explain the advantages of PLC over Relay
- 2.2 Draw the PLC ladder diagram for Motor forward-reverse with mutual interlock
- 2.3 Explain about PLC output group register
- 2.4 List the types of counters and explain any one
- 2.5 Explain PLC multiplication function with example
- 2.6 Write the difference between SKIP and MCR function
- 2.7 Explain the function which eliminates the effect of spikes from contact bounce.
- 2.8 Explain PLC input module with neat sketch.

3.0 ANSWER ANY FOUR OF THE FOLLOWING

4*4=16

- 3.1 Explain each part of PLC with the block diagram
- 3.2 Write a program for START-STOP -JOG.
- 3.3 Mention different types of timers based on inputs and explain each with example
- 3.4 Explain block transfer function in PLC
- 3.5 Explain PLC DRUM function with an example
- 3.6 List the factors considered while selecting a PLC

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN MECHATRONICS ENGINEERING & SMART FACTORY – CP15
IV SEMESTER SUPPLEMENTARY EXAMINATION-JULY 2023

Subject: Industrial Electronics
Subject Code: CP150401

Time: 2 Hr.
Marks: 50

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING

2*8=16

- 1.1 List out any four PPEs
- 1.2 Describe Power Diode
- 1.3 Define softness factor.
- 1.4 List out some of the controlled power devices.
- 1.5 Draw single phase half wave rectifier circuit.
- 1.6 Write short notes on firing angle or triggering angle of an SCR.
- 1.7 List out the types of DC-DC converters.
- 1.8 Write a short notes about snubber circuit
- 1.9 Give the concept of thermal resistance.
- 1.10 Write short notes on EMC

2.0 ANSWER ANY SIX OF THE FOLLOWING

3*6=18

- 2.1 Write the first aid steps taken when a person got heart attack.
- 2.2 Define reverse recovery time.
- 2.3 Draw the symbol of POWER MOSFET and name its terminals
- 2.4 Define Holding & Latching current
- 2.5 What do you mean by duty cycle?
- 2.6 Write the importance of heat sink in a circuit.
- 2.7 Draw the block diagram of DC Drive.
- 2.8 With a neat sketch explain about linear power supplies.

3.0 ANSWER ANY FOUR OF THE FOLLOWING

4*4=16

- 3.1 Explain the term 5S.
- 3.2 List out the applications of power electronics.
- 3.3 Draw and explain the switching characteristics of power BJT
- 3.4 Explain the function of freewheeling diode in rectifier.
- 3.5 Explain the working of buck converter with the help of a neat diagram
- 3.6 Explain about PMDC motor with neat sketch.

