

NETTUR TECHNICAL TRAINING FOUNDATION
DIPLOMA IN ELECTRICAL & ELECTRONICS ENGINEERING – CP23
V SEMESTER REGULAR & SUPPLEMENTARY EXAMINATION-JAN 2023

Subject: Power Electronics-I
Subject Code: CP23503T

Total Time: 2 Hr.
Total Marks: 50 Marks

PART B

1.0 ANSWER ANY EIGHT OF THE FOLLOWING **2*8=16**

- 1.1 What are the types of power transistor?
- 1.2 What is the difference between BJT and MOSFET?
- 1.3 What is Snubber circuit?
- 1.4 Name the heat transfer techniques.
- 1.5 Draw the block diagram of linear power supply
- 1.6 Define power electronics & Write any 2 applications of power electronics
- 1.7 What do you understand by ripple factor?
- 1.8 What is commutation?
- 1.9 Draw the symbols for components a) BY229 b) IRF540.
- 1.10 Define Chopper

2.0 ANSWER ANY SIX OF THE FOLLOWING **3*6=18**

- 2.1 What is the difference between linear and power electronics?
- 2.2 What are the different methods to turn on the SCR?
- 2.3 Define a) duty cycle b) softness factor c) form factor
- 2.4 What is phase controlled rectifier and its types
- 2.5 Write the full form and draw the symbols a) GTO b) IGBT c) SCR
- 2.6 Write the difference between controlled and uncontrolled rectifier
- 2.7 Define a) Latching current b) Holding current
- 2.8 Draw the VI Characteristics of power diode.

3.0 ANSWER ANY FOUR OF THE FOLLOWING **4*4=16**

- 3.1 Write down the control strategies of chopper
- 3.2 Draw and explain the working of boost convertor
- 3.3 Explain three phase half wave rectifier circuit with neat diagram
- 3.4 Define Thyristor and explain its modes of operations
- 3.5 Explain reverse recovery characteristics of power diode with proper diagram
- 3.6 What is di/dt in SCR? How SCR can be protected from this?

